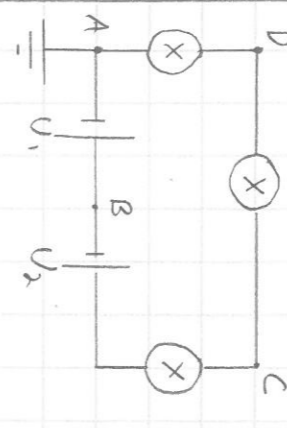
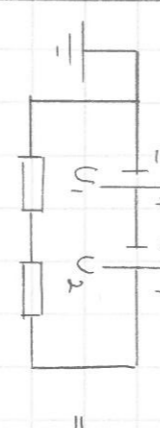
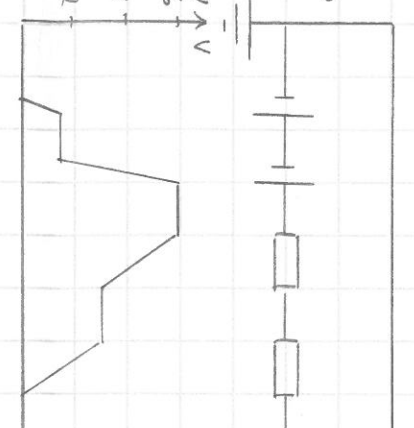


5.12 $\lambda = 7,0 \text{ cm}$, $E = 4,7 \frac{\text{eV}}{\text{mm}}$
 $U = E \lambda = 4,7 \frac{\text{eV}}{\text{mm}} \cdot 70 \text{ mm} = 329 \text{ eV} \approx 330 \text{ eV (realitään)}$



6.6 a) $Q = I \cdot t$ $I: I$
 $\Rightarrow t = \frac{Q}{I} = \frac{12000 \text{ mAh}}{330 \text{ mA}} \approx 36,3636 \text{ h} \approx 36 \text{ h}$
 b) $I = \frac{Q}{t} = \frac{\text{mC}}{\text{s}}$ $\Rightarrow I = \frac{10 \text{ A} \cdot 1 \text{ h}}{1,60218 \cdot 10^{-19} \text{ C}} \approx 6,24150 \cdot 10^{18}$
 $I = \frac{Q}{t} = \frac{\text{mC}}{\text{s}}$ $\Rightarrow I = \frac{1,60218 \cdot 10^{-19} \text{ C}}{1,60218 \cdot 10^{-19} \text{ s}} \approx 6,2 \cdot 10^{18}$


6.7 $Q = 4500 \text{ mAh}$
 a) $Q = 4500 \cdot 10^{-3} \text{ A} \cdot 60 \cdot 60 \text{ s} = 16200 \text{ C} \approx 16000 \text{ C}$
 b) $Q = m \cdot e$ $\Rightarrow m = \frac{Q}{e} = \frac{16200 \text{ C}}{1,60218 \cdot 10^{-19} \text{ C}} \approx 1,01112 \cdot 10^{23} \approx 1,0 \cdot 10^{23}$
 c) $0,25 \text{ Q} = I \cdot t$ $I: I$
 $\Rightarrow I = \frac{0,25 \text{ Q}}{t} = \frac{0,25 \cdot 4500 \text{ mAh}}{3,0 \text{ h}} = 375 \text{ mA} \approx 0,38 \text{ A}$

7.11 
 $U_1 = U_2 = 4,5 \text{ V}$
 a) $U_{BA} = U_B - U_A = U_1 = 4,5 \text{ V}$
 b) Rücklicht 2.
 $U_1 + U_2 - U - U = 0$
 $\Rightarrow U = \frac{U_1 + U_2}{3} = \frac{4,5 \text{ V} + 4,5 \text{ V}}{3} = 3,0 \text{ V}$
 $U_{DA} = U_D - U_A = U = 3,0 \text{ V}$

7.14 
 $U_1 = 1,5 \text{ V}$ $U_2 = 4,5 \text{ V}$
 $K2: \sum \Delta V = U_1 + U_2 - U - U = 0$
 $\Rightarrow U = \frac{U_1 + U_2}{2} = 3,0 \text{ V}$


8.7 $I = 2 \text{ mA}$, $U = 12 \text{ V}$
 Ohm's law: $U = R \cdot I \Rightarrow R = \frac{U}{I} = \frac{12 \text{ V}}{0,002 \text{ A}} = 6000 \Omega$

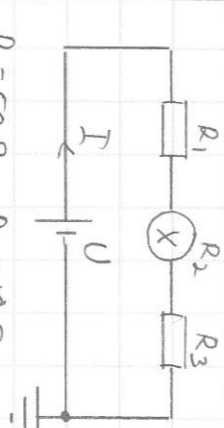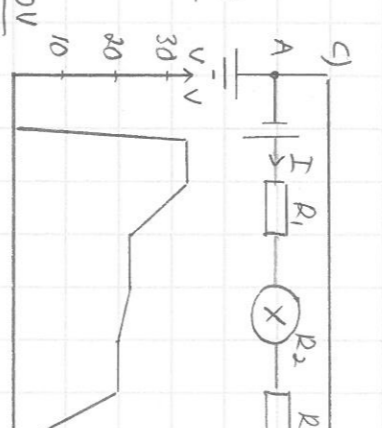8.15 
 $R_1 = 50 \Omega$, $R_2 = 10 \Omega$
 $R_3 = 100 \Omega$, $I = 0,20 \text{ A}$
 a) $U_1 = R_1 \cdot I = 50 \Omega \cdot 0,20 \text{ A} = 10 \text{ V}$
 $U_3 = R_3 \cdot I = 100 \Omega \cdot 0,20 \text{ A} = 20 \text{ V}$
 b) $U = R_1 \cdot I + R_2 \cdot I + R_3 \cdot I = (50 \Omega + 10 \Omega + 100 \Omega) \cdot 0,20 \text{ A} = 32 \text{ V}$

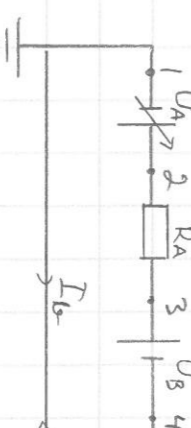
8.17 
 $R_A = 220 \Omega$
 $R_B = 330 \Omega$
 $U_B = 3,0 \text{ V}$
 a) $U_A = 6,0 \text{ V}$
 $K2: \sum \Delta V = U_A - I R_A - U_B - I R_B = 0$
 $\Rightarrow I = \frac{U_A - U_B}{R_A + R_B} = \frac{6,0 \text{ V} - 3,0 \text{ V}}{220 \Omega + 330 \Omega} \approx 0,00545455 \text{ A}$
 $V_1 = 0 \text{ V}$ (maadotus)
 $V_2 = V_1 + U_A = 0 \text{ V} + 6,0 \text{ V} = 6,0 \text{ V}$
 $V_3 = V_2 - R_A \cdot I = 6,0 \text{ V} - 220 \Omega \cdot 0,00545455 \text{ A} = 4,8 \text{ V}$
 $V_4 = V_3 - U_B = 4,8 \text{ V} - 3,0 \text{ V} = 1,8 \text{ V}$
 $V_5 = 0 \text{ V}$ (maadotus)

b) $U_A = 1,5 \text{ V}$
 $K2: I = \frac{U_A - U_B}{R_{20} + 330 \Omega} \approx -0,00272727 \text{ A}$
 $I < 0 \Rightarrow I_B$: toisen suunnan kuin I_A
 $V_1 = 0 \text{ V}$
 $V_2 = 1,5 \text{ V}$
 $V_3 = V_2 + R_A \cdot I = 1,5 \text{ V} + 220 \Omega \cdot 0,00272727 \text{ A} = 2,1 \text{ V}$
 $V_4 = V_3 - U_B = 2,1 \text{ V} - 3,0 \text{ V} = -0,9 \text{ V}$
 $V_5 = 0 \text{ V}$

9.7 $R_{20} = 6,0 \Omega$, $\alpha = 4,84 \cdot 10^{-3} \frac{1}{\text{C}}$, $t = 2100 \text{ C}$
 $R = R_{20} (1 + \alpha \Delta t) = 6,0 \Omega (1 + 4,84 \cdot 10^{-3} \frac{1}{\text{C}} \cdot (2100 \text{ C} - 20 \text{ C}))$
 $\approx 66,4032 \Omega \approx 66 \Omega$

9.8 $S = 2,655 \cdot 10^{-8} \Omega \text{ m}$
 a) $R = \frac{\rho}{A} \cdot l = 2,655 \cdot 10^{-8} \Omega \text{ m} \cdot \frac{12000 \text{ m}}{0,25 (0,01 \text{ m})^2} = 12,744 \Omega \approx 13 \Omega$
 b) $\frac{R_2}{R} = \frac{\frac{\rho}{A_2} \cdot l_2}{\frac{\rho}{A} \cdot l} = \frac{A}{A_2} = \frac{l}{l_2} \Rightarrow A_2 = 2 \text{ A} = 2 \cdot 0,25 \text{ cm}^2 = 0,50 \text{ cm}^2$
 c) $U = R \cdot I = S \frac{l}{A} \cdot I = 2,655 \cdot 10^{-8} \Omega \text{ m} \cdot \frac{1000 \text{ m}}{\pi \cdot (4,9 \cdot 10^{-3} \text{ m})^2} \cdot 12 \text{ A}$
 $\approx 1,7461052 \cdot 12 \text{ A} \approx 20,9532 \text{ V} \approx 21 \text{ V}$

9.14 $l_1 = 1,1 \text{ m}$; $d = 0,36 \text{ mm}$; $R_1 = 13 \Omega$; $l_2 = 3,5 \text{ m}$
 $\frac{R_2}{R_1} = \frac{\frac{\rho}{A} \cdot l_2}{\frac{\rho}{A} \cdot l_1} = \frac{l_2}{l_1} \cdot R_1$
 $\Rightarrow R_2 = \frac{l_2}{l_1} \cdot R_1 = \frac{3,5 \text{ m}}{1,1 \text{ m}} \cdot 13 \Omega \approx 41,3636 \Omega \approx 41 \Omega$

10.7 a) $P = U \cdot I \Rightarrow I = \frac{P}{U} = \frac{18 \text{ W}}{12 \text{ V}} = 1,5 \text{ A}$
 b) $I = \frac{P}{U} = \frac{535 \text{ W}}{230 \text{ V}} \approx 2,32609 \text{ A} \approx 2,3 \text{ A}$

10.8 $P = U \cdot I = U \cdot \frac{U}{R} = \frac{U^2}{R}$
 a) $P = \frac{(4,5 \text{ V})^2}{4,0 \Omega} = 5,0625 \text{ W}$
 b) $P = \frac{(4,5 \text{ V})^2}{6,0 \Omega} = 3,375 \text{ W}$
 c) $P = \frac{(9,0 \text{ V})^2}{1,5 \Omega} = 54 \text{ W} \leftarrow$ suurin teho \Rightarrow riskein
 d) $P = \frac{(9,0 \text{ V})^2}{7,0 \Omega} \approx 11,5714 \text{ W}$

10.12 $P = 1800 \text{ W}$, $U = 230 \text{ V}$, $I_{\text{max}} = 10 \text{ A}$
 a) $P = U \cdot I \Rightarrow I = \frac{P}{U} = \frac{1800 \text{ W}}{230 \text{ V}} \approx 7,82609 \text{ A} \approx 7,8 \text{ A}$
 b) Sulake kestää tohon:
 $P_{\text{max}} = U \cdot I_{\text{max}} = 230 \text{ V} \cdot 10 \text{ A} = 2300 \text{ W}$
 kestäväiden kestoarvot: $1800 \text{ W} + 800 \text{ W} = 2600 \text{ W} > P_{\text{max}}$
 \Rightarrow ei voi käyttää

10.17 $P = 3,2 \text{ kW}$, $t = 31,7 \text{ h}$
 Muuttamispunktin lämpöteoreettinen energia:
 $E = P \cdot t = 3,2 \text{ kW} \cdot 31,7 \text{ h} = 634,4 \text{ kWh} < 780 \text{ kWh}$
 \Rightarrow kestää
 Säästö: $780 \text{ kWh} \cdot x = 110 \text{ e}$
 $\Rightarrow x = \frac{110 \text{ e}}{780 \text{ kWh}} \approx 0,141026 \frac{\text{e}}{\text{kWh}} \approx 0,14 \frac{\text{e}}{\text{kWh}}$

11.5 a) $R = R_1 + R_2 + R_3 = 20 \Omega + 30 \Omega + 35 \Omega = 85 \Omega$
 b) $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$ $| ()^{-1}$
 $\Rightarrow R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{\frac{1}{20 \Omega} + \frac{1}{30 \Omega}} = 12 \Omega \approx 10 \Omega$