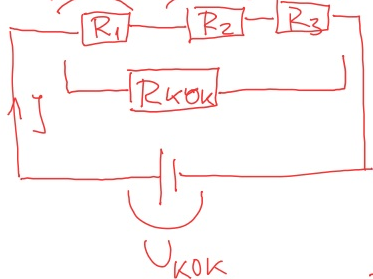


## Vertusten kytkennät

Sarjaankytkentä:  
 $U_1 = R_1 J$   $U_2 = R_2 J$   $U_3 = R_3 J$




$$(kII) \quad \left. \begin{aligned} U_{kok} &= U_1 + U_2 + U_3 \\ U_{kok} &= R_{kok} J \end{aligned} \right\} \Rightarrow$$

$$R_{kok} J = R_1 J + R_2 J + R_3 J \quad | : J$$

$$\boxed{R_{kok} = R_1 + R_2 + R_3}$$

Rinnankytkentä:

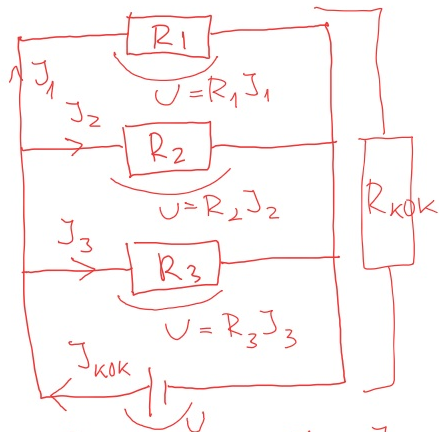


$$(kI) \quad J_{kok} = J_1 + J_2 + J_3$$

$$\frac{U}{R_{kok}} = \frac{U}{R_1} + \frac{U}{R_2} + \frac{U}{R_3} \quad || : U$$

$$\boxed{\frac{1}{R_{kok}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

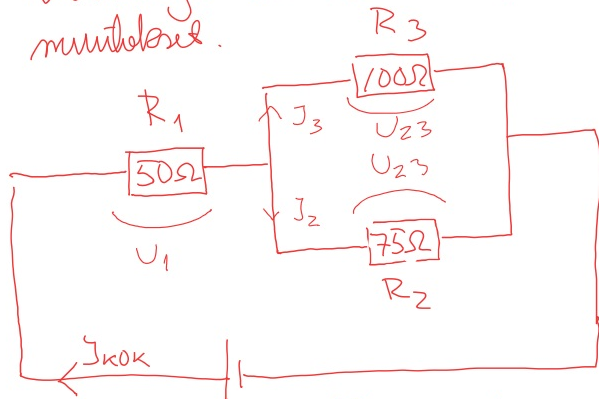Esim. Lasketaan vastusten läpi kulkevat virrat ja vastuksilla tapahtuvat potentiaali-  
muutokset.



$$9,0\text{V} = U_{\text{kok}}$$

$$\begin{aligned} \text{(kII)} \quad U_{\text{kok}} &= U_1 + U_{23} \\ &= R_1 J_{\text{kok}} + R_{23} J_{\text{kok}} \end{aligned}$$

Piirin kokonaisresistanssi

$$R_{\text{kok}} = R_1 + R_{23}$$

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} \Leftrightarrow \frac{1}{R_{23}} = \frac{1}{75} + \frac{1}{100} \Leftrightarrow R_{23} = \frac{1}{\frac{1}{75} + \frac{1}{100}} = 42,85\Omega$$

$$R_{\text{kok}} = 50\Omega + 42,85\Omega = 92,85\Omega$$

$$J_{\text{kok}} = \frac{U_{\text{kok}}}{R_{\text{kok}}} = \frac{9,0\text{V}}{92,85\Omega} = 0,0969\text{A} \approx 97\text{mA}$$

$$U_1 = 50\Omega \cdot 0,0969\text{A} = 4,846\text{V} \approx 4,8\text{V}$$

$$U_{23} = 42,85\Omega \cdot 0,0969\text{A} = 4,153\text{V} \approx 4,2\text{V}$$

$$J_2 = \frac{U_{23}}{R_2} = \frac{4,153\text{V}}{75\Omega} = 0,05538\text{A} \approx 55\text{mA}$$

$$J_3 = \frac{U_{23}}{R_3} = \frac{4,153\text{V}}{100\Omega} = 0,04153\text{A} \approx 42\text{mA}$$